

Part A  
Part B

1. There are four things required to make use of electricity: \_\_\_\_\_, \_\_\_\_\_, \_\_\_\_\_, and \_\_\_\_\_.
2. Draw a simple diagram of a circuit where a battery is connected to a light globe.

3. Describe why the light globe in the circuit shown on the right is not on.

---



---



---



Part C

4. Draw a circuit diagram (using circuit symbols) of a circuit that has a switch which switches on one light globe.

Part D

## LIGHT GLOBES IN SERIES

5. (a) Draw a circuit diagram of a circuit where a battery powers two light globes that are connected in series.  
(b) Draw a second circuit diagram that includes a switch so that the two light globes connected in series can be turned on and off.

6. If one light globe in the circuits above suddenly blows, why will the other one also go out?

---



---

7. How does the amount of light emitted by the two globes in the circuit above compare to the amount of light that would be emitted if just one of the globes was connected to the battery?

---



---

## LIGHT GLOBES IN PARALLEL

8. (a) Draw a circuit diagram of a circuit where a battery powers two light globes that are connected in parallel.  
(b) Draw a second circuit diagram that includes a switch so that the two light globes connected in parallel can be turned on and off.

9. If one light globe in the circuits in Q8 suddenly blows, how will the other one be affected? Explain.
- 
- 
10. How does the amount of light emitted by the two globes in the circuit in Q8 compare to the amount of light that would be emitted if just one of the globes was connected to the battery?
- 
- 
11. Draw a circuit diagram of a circuit where one switch switches on one light globe and the other switch switches on another light globe.

### CRITICAL-THINKING EXERCISES

12. Describe the operation of the circuits on the right. (You can refer to each component as switch A, light globe C etc). Eg. When switch A is pressed... (The circuits are not necessarily well constructed!)

(a) \_\_\_\_\_

(b) \_\_\_\_\_

(c) \_\_\_\_\_

(d) \_\_\_\_\_

13. Which globes in the circuit on the right will remain lit in the following circumstances? (There may be none)

(a) Globe B blows (or is removed). \_\_\_\_\_

(b) Globe C blows. \_\_\_\_\_

(c) Globes B and D blow. \_\_\_\_\_

(d) Globes A and B blow. \_\_\_\_\_

14. Points A-E are points in the circuit where switches can be placed.

Where would you place a single switch so that

(a) all light globes can be turned on and off at the same time? \_\_\_\_\_

(b) light globe 2 can be turned off and on while the others stay on? \_\_\_\_\_

(c) light globes 2 and 3 can be turned on and off at the same time (while light globe 1 remains on)? \_\_\_\_\_

15. If you had two switches, where would you place them so that light globe 1 can be switched on and off with one switch and light globes 2 and 3 can be switched on and off with the other?

\_\_\_\_\_

